

# Flashlight - Activity Guide



What are a few items that rely on circuits to function?

\_\_\_\_\_

Circle which way (or both) that the electrical current will flow?  
Remember, it takes the path of least resistance.

